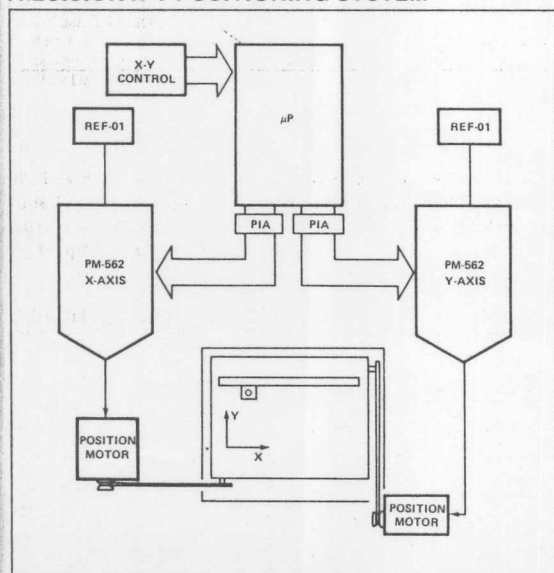


**NOTES:**


1. Calibration Procedure: Set  $V_{REF} = 10.0000V$ . Next set digital inputs  $B_1$  thru  $B_{12}$  to digital zero and adjust  $R_1$  until  $V_{OUT} = -10.0000V$ . Set digital inputs  $B_1$  thru  $B_{12}$  to 1000 0000 0000 (i.e. only turn ON MSB) and adjust  $R_2$  until  $V_{OUT} = 0.0000V$ .
2. Bypass  $V+$  and  $V-$  supplies with a  $0.01\mu F$  in parallel with  $1\mu F$  capacitors.

**FIGURE 3:  $\pm 10\text{V}$  Bipolar Voltage Output**


## PRECISION X-Y POSITIONING SYSTEM




## 4-20mA TRANSMITTER

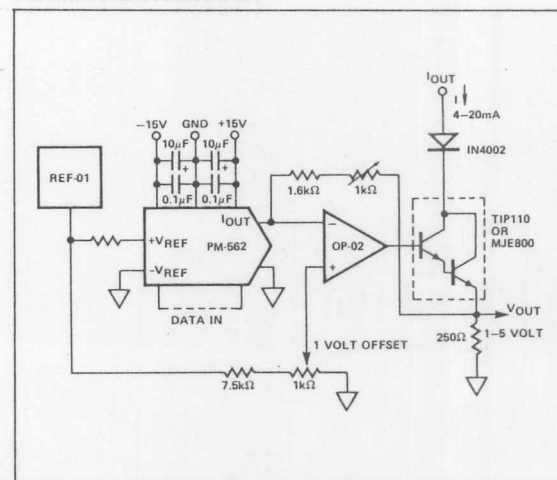

# APPLICATIONS INFORMATION

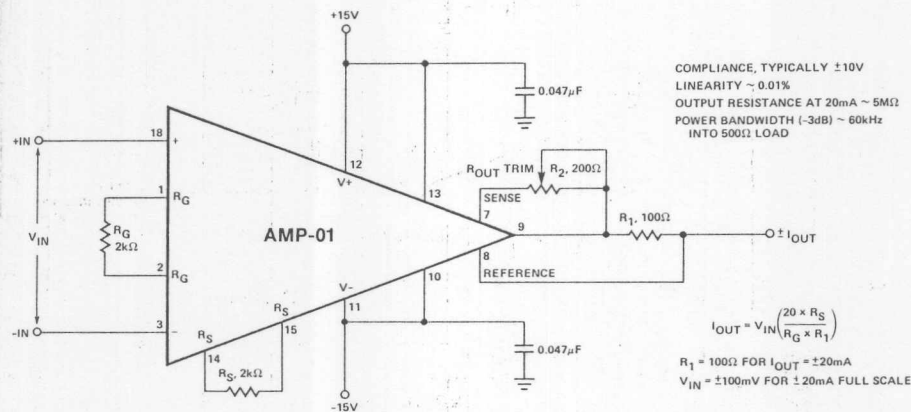

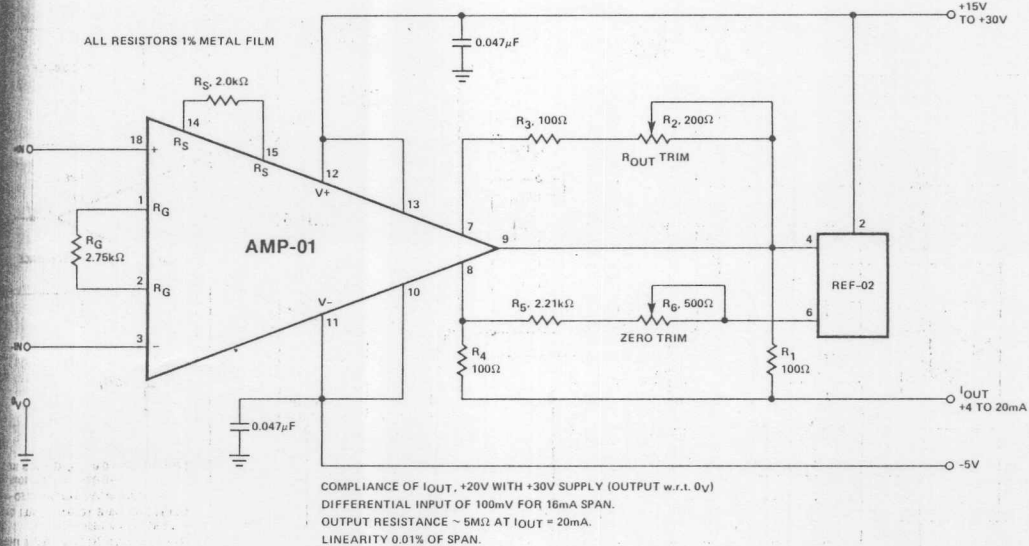
7. High-compliance bipolar current source with 13-bit linearity.




8. 13-bit linear 4-20mA transmitter constructed by adding a voltage reference. Thermocouple signals can be accepted without preamplification.

# AMP-01 LOW-NOISE PRECISION INSTRUMENTATION AMPLIFIER

## FORMATION

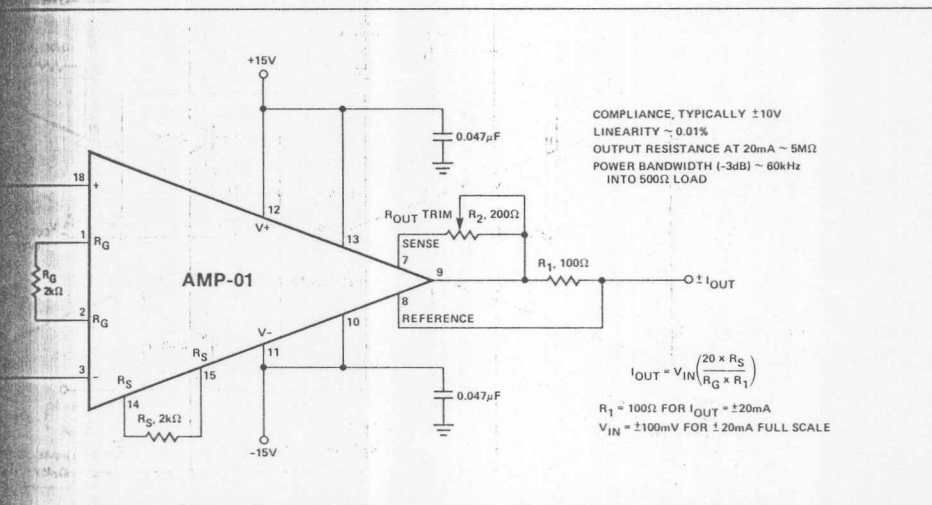

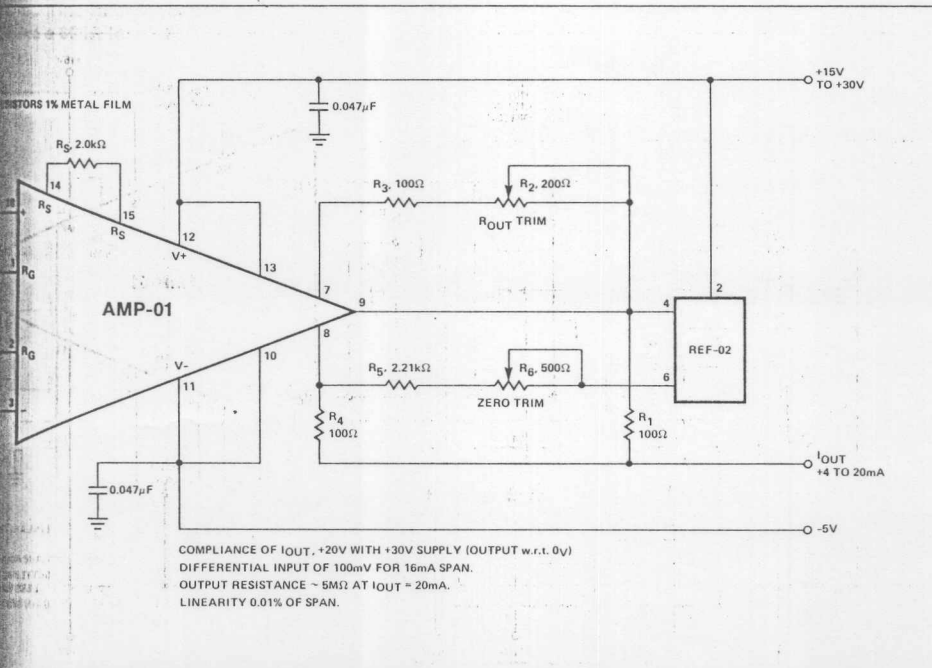precision bipolar current source with 13-bit linearity.



4-20mA transmitter constructed by adding a voltage reference. Thermocouple signals can be accepted and amplified.

INSTRUMENTATION AMPLIFIERS

6



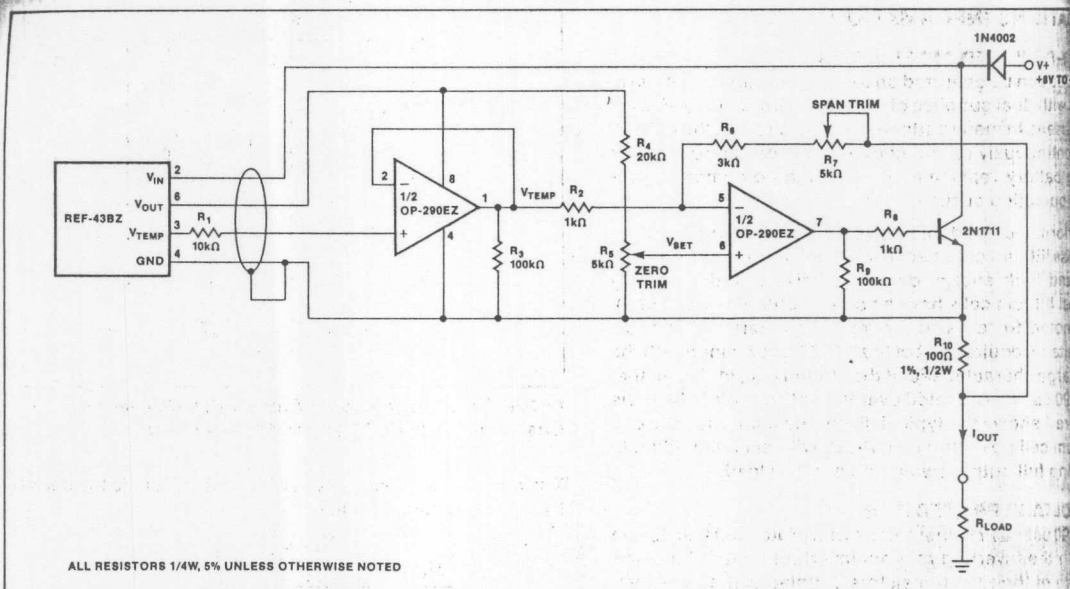


FIGURE 2: Temperature to 4-20mA Transmitter

### VARIABLE SLEW RATE FILTER

The circuit shown in Figure 3 can be used to remove pulse noise from an input signal without limiting the response rate to a genuine signal. The non-linear filter has use in applications where the input signal of interest is known to have physical limitations. An example of this is a transducer output where a change of temperature or pressure cannot exceed a certain rate due to physical limitations of the environment. The filter consists of a comparator which drives an integrator. The comparator compares the input voltage to the output voltage and forces the integrator output to equal the input voltage.  $A_1$  acts as a comparator with its output high or low. Diodes  $D_1$  and  $D_2$  clamp the voltage across  $R_3$  forcing a constant current to flow in or out of  $C_2$ .  $R_3$ ,  $C_2$  and  $A_2$  form an integrator with  $A_2$ 's output slewing at a maximum rate of:

$$\text{Maximum slew rate} = \frac{V_D}{R_3 C_2} \approx \frac{0.6V}{R_3 C_2}$$

For an input voltage slewing at a rate under this maximum slew rate, the output simply follows the input with  $A_1$  operating in its linear region.

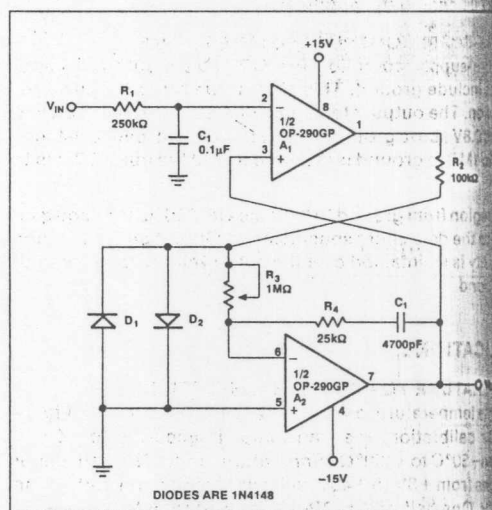
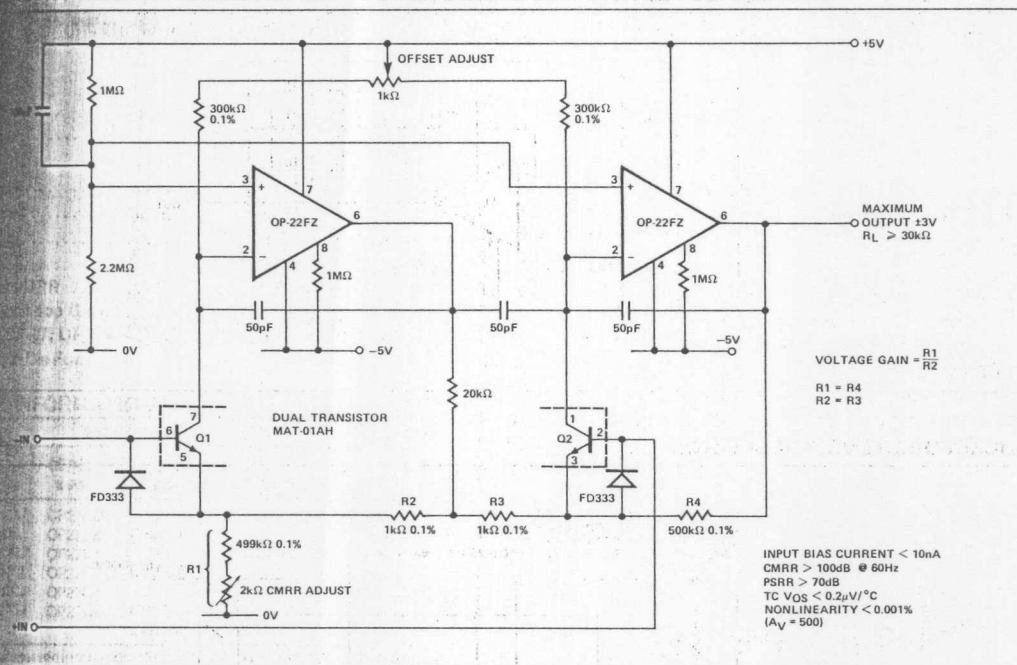


FIGURE 3: Variable Slew Rate Filter

INSTRUMENTATION AMPLIFIER — POWER DRAIN  $\leq 3\text{mW}$  WITH  $\pm 5\text{V}$  SUPPLIES

the OP-22 is used as a gated amplifier where consumption and bandwidth are controllable.  $R_S$  can be used for a specific lower-power operation or omitted so the amplifier can be completely shut down.

A low-power instrumentation amplifier that consumes less than  $3\text{mW}$  with  $\pm 5\text{V}$  supplies is shown in Figure 3. Offset drift is less than  $0.2\mu\text{V}/^\circ\text{C}$  and common-mode rejection is  $\pm 3\text{V}$  with CMRR of over  $100\text{dB}$  at  $60\text{Hz}$ .

Control systems use two-wire 4-20mA current transmitters when sending analog signals through noisy environments. The "zero" or "offset" current of  $4\text{mA}$  may be used to condition the transmitter signal conditioning amplifiers and/or the transducer. This allows remote signal conditioning without having a remote power source. Power is provided at the receiving end where the signal current is monitored by a  $50\Omega$  resistor. The 4-20mA transmitter shown in Figure 4 has high stability, excellent linearity, and generates a  $4\text{mA}$  current output. A  $5\text{V}$  reference is available for the transducers and micropower amplifiers at a maximum current of  $2\text{mA}$ .

## TWO TERMINAL 4-20mA TRANSMITTER

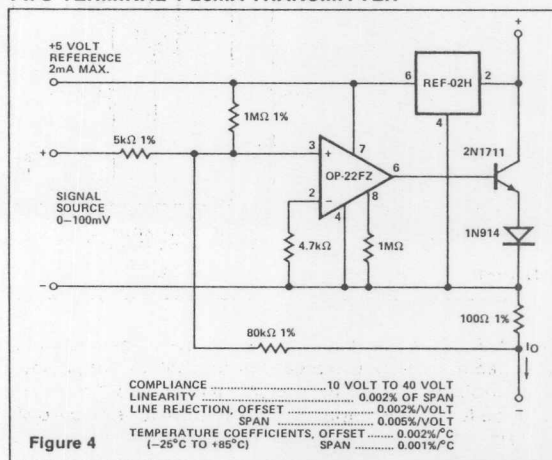


Figure 4




age to 400μV, providing high nulling performance. **TEMPERATURE RANGE** The OP-90's input offset voltage is true "zero" over this level, a low level to pull the output

he OP-90 has an on. Output has entire voltage

**REFERENCE** powered voltage. At this r 18 months of the reference range n at 120μV. n the bandw ludes unequal match creake 3 wh In the vol cross added to the coefficient e Reference

0.1V 0.2V

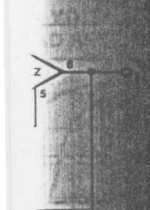


at 25°C produces minimum drift over temperature. references can have start-up problems. With R1 and R2, the OP-90 is beyond its positive input range and has an undefined output state. Shorting Pin 5 (offset pin) to ground forces the output high under power and insures reliable start-up without significantly affecting the OP-90's offset drift.

**SINGLE OP-AMP FULL-WAVE RECTIFIER**

This is a full-wave rectifier circuit that provides the output of input signals up to ±2.5V even though it is powered by a single 5V supply. For negative inputs, the output is an unity gain inverter. Positive signals force the output to ground. The 1N914 diode becomes forward biased and the signal passes through R1 and R2 to the output. The output impedance is dependent on input impedances cause an asymmetric output. For high impedances, this can be corrected by reducing the input impedances or heavy loads can be buffered by a second op-amp. Figure 6 shows the output of the full-wave rectifier with a 10Hz input signal.

Single Op-Amp Full Wave Rectifier

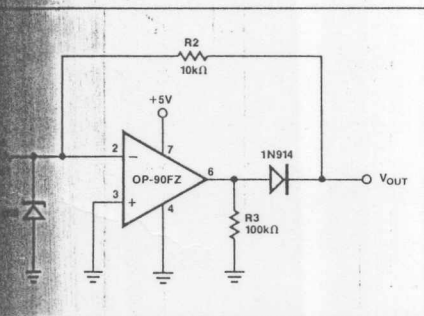

Two Wire 4-20mA Transmitter


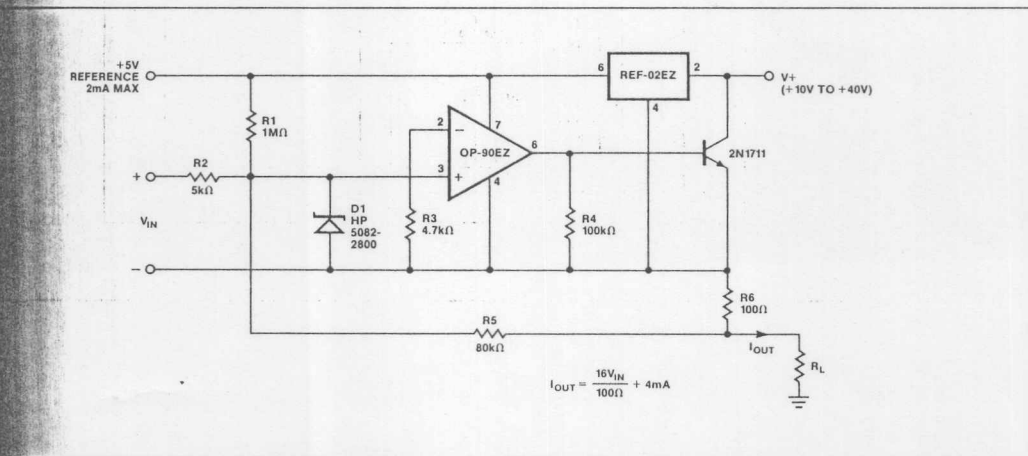


FIGURE 6: Output of Full-Wave Rectifier With 4Vp-p, 10Hz Input

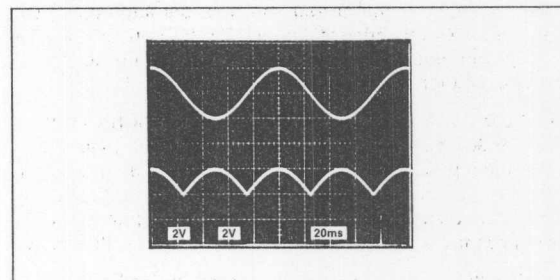

**TWO WIRE 4-20mA CURRENT TRANSMITTER**

The current transmitter of Figure 7 provides an output of 4mA to 20mA that is linearly proportional to the input voltage. Linearity of the transmitter exceeds 0.004% and line rejection is 0.0005%/volt.

Biasing for the current transmitter is provided by the REF-02EZ. The OP-90EZ regulates the output current to satisfy the current summation at the noninverting node:

$$I_{OUT} = \frac{1}{R_6} \left( \frac{V_{IN} R_5}{R_2} + \frac{5V R_5}{R_1} \right)$$

For the values shown in Figure 7,

$$I_{OUT} = \left( \frac{16}{100\Omega} \right) V_{IN} + 4mA$$

giving a full-scale output of 20mA with a 100mV input. Adjustment of R2 will provide an offset trim and adjustment of R1 will provide a gain trim. These trims do not interact since the noninverting input of the OP-90 is at virtual ground. The Schottky diode, D1, prevents input voltage spikes from pull-

5  
OPERATIONAL AMPLIFIERS / BUFFERS